

LA5685N

Multi-function, multi-power supply IÇ for car radios


OVERVIEW

The LA5685N is a multi-function, multi-power supply IC developed for car radios. It has 8.5V AM output, 8.5V FM output, 8.5V common output, 5.2V microcomputer output, and 5.1V bias output, making it the ideal power supply for LA1833 and LA1887 ICs for FM/AM tuner systems.

FEATURES


- A total of five built-in outputs: V₁=8.5 V
 (AM), V₂=8.5 V (FM), V₃=8.5 V (common),
 V₄=5.2 V (microcomputer), and V₅=5.1 V
- R ON/OFF, FM/AM switching functions
- Minimal static current for back up (120 μA typ.)
- Built-in overvoltage protection circuit (V₁, V₂, and V₃ go off at 28 V (typ.), V₄ and V₅ go off at 56 V (typ.))
- Built-in thermal shutdown circuit (output goes off at Tj = 170°C (typ.))
- Built-in short protection circuit

Pinout

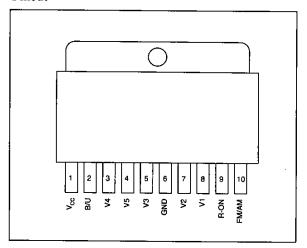

Package Dimensions


Unit: mm 3046B-SIP10F

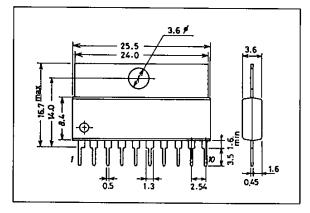


LA5685N

Maximum Ratings / Ta = 25	i°C					unit	
Input voltage		cl 4% duty pulse width 200 mS puls	e input	75		V	
		alse when output on)	o input	7.5		•	
	V _{CC} max			25		V	
Output current	II max			80		mA	
, p	I2 max			100		mA	
	I3 max			200		mA	
	I4 max			50		mA	
	I5 max			5		mA	
Allowable power dissipa				2.45		W	
		Topr		-35~+85		°C	
Storage temperature	Tstg			-40~+125		°Č	
Operating Conditions / Ta=	25°C					unit	
Power supply voltage	V _{CC} op	9 V~10.5 V not regulated	(9~16		V	
B/U voltage	B/U	6 V~8.5 V not regulated	6~16 V				
Operating Characteristics	External 33µF O	s otherwise noted, V _{CC} = 12V, R-ON: S capacitor connected to V1, V2, V3,	and V4				
a	X	B 011 B 411 1 011	min	typ	max		Note
Static current	I _{CC} 1	R-ON=FM/AM=0V	•	4.5	7.0	mA	
0	$I_{CC}2$	R-ON=FM/AM=5V		4.5	7.0	mA	
Output voltage	V1	FM/AM = 0V, I1 = 20mA	7.8	8.5	9.2	V	
	V2	FM/AM=5V,I2=50mA	7.8	8.5	9.2	V	•
	V3	I3=100mA	7.8	8.5	9.0	V	
	V4	I4=20mA	4.9	5.2	5.5	V	
4.7	V5	I5=1mA	V4-0.5		V4	V	
Line regulation	△V1 line	FM/AM=0V,11 <v<sub>CC<15V, I1=20mA</v<sub>			50	mV	
	△V2 line	FM/AM=5V,11V <v<sub>CC<15V, I2=50mA</v<sub>			50	mV	
	△V3 line	$I3 = 100 \text{mA}, 11 \text{V} < \text{V}_{CC} < 15 \text{V}$			50	mV	
	△V4 line	I4=20mA,11V <v<sub>CC<15V</v<sub>			50	mV	
	△V5 line	$I5 = 1 \text{ mA}, 11 \text{ V} < \text{V}_{CC} < 15 \text{ V}$			50	mV	
B/U static current	IB/U	$B/U = 16V, V_{CC} = 0V$			0.3	mA	
V5 On-Off TH voltage	$V5_{TH}$	B/U=12V	6	7	8	V	
R-ON on voltage	R-ON ON		2.5		V_{CC}	V	
R-ON off voltage	R-ON OFF		-0.3		+1.0	V	
FM/AM on voltage	FM/AM ON		2.5		V_{CC}	V	
FM/AM off voltage	FM/AM OFF		-0.3		+1.0	V	
Input current R-ON	IR-ON	R-ON=5V			0.2	mΑ	•
Input current FM/AM	IFM/AM	FM/AM=5V			0.2	mA	
Load regulation	△V1 Load	FM/AM=0V,1mA <i1<65ma< td=""><td></td><td></td><td>50</td><td>mV</td><td></td></i1<65ma<>			50	mV	
	△V2 Load	FM/AM = 5V, 1mA < I2 < 90mA			50	mV	
	△V3 Load	1mA <i3<160ma< td=""><td></td><td></td><td>100</td><td>mV</td><td></td></i3<160ma<>			100	mV	
	△V4 Load	ImA <i4<40ma< td=""><td></td><td></td><td>50</td><td>mV</td><td></td></i4<40ma<>			50	mV	
Ripple regulation	△V5 Load	0.1mA<15<2mA	40		200	mV	\ & /
	Rr1	FM/AM=0V, f=120Hz, I1=20mA				dB	*
	Rr2	FM/AM=5V, f=120Hz, I2=50mA				dB	*
	Rr3	f=120Hz, I3=100mA	40			dB	*
	Rr4	f=120Hz, I4=20mA	40			dB	*
	Rr5	f = 120Hz, $I5 = 1$ mA	40			dB	*

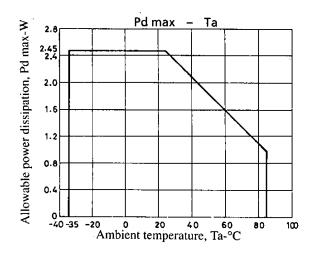Note: * indicates design guaranteed value.




Block Diagram

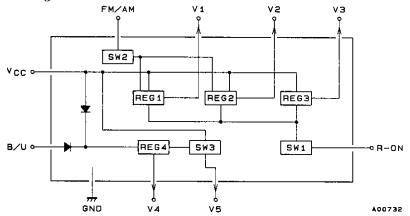


Pin	Name	Pin	Name		
1	V_{CC}	6	GND		
2	B/U	7	V2		
3	V4	8	VI		
4	V5	9	R-ON		
5	V3	10	FM/AM		

Measurement Circuit

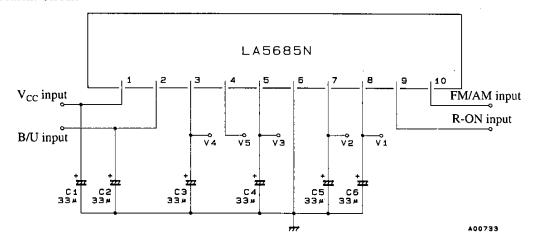

Unit (capacitance: F)

Application Circuit Examples

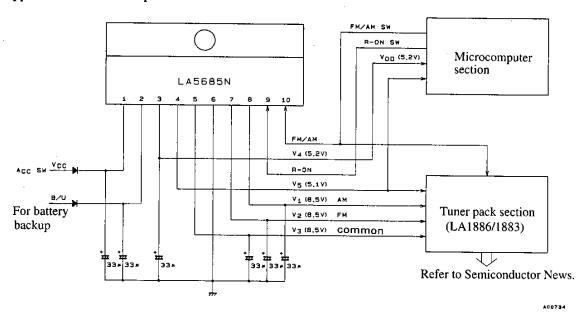

Input/Output Table

Inputs			Outputs					
A _{CC}	B/U	R-ON	FM/AM	V1	V2	V3	V4	V5
L	L	*	*	L	L	L	L	L
L	Н	*	*	L	L	L	H	L
Н	*	Н	L	Н	L	Н	н	Н
Н	*	Н	Н	L	н	Н	н	Н
Н	*	L	*	L	L	L	н	Н

- Negative voltages are not to be applied to these pins.
- Always use input/output capacitors (instead of for V5).
 (We recommend OS capacitors with good characteristics at low temperature.)
- Built-in overvoltage protection circuit (V1, V2, and V3 go off at 28V (typ.), V4 and V5 go off at 56V (typ.))
- Built-in thermal shutdown circuit (output goes off at T_i = 170°C (typ.)
- Built-in short protection circuit
 - No products described or contained herein are intended for use in surgical implants, life-support systems, aerospace equipment, nuclear power control systems, vehicles, disaster/crime-prevention equipment and the like, the failure of which may directly or indirectly cause injury, death or property loss.
 - Anyone purchasing any products described or contained herein for an above-mentioned use shall:
 - ① Accept full responsibility and indemnify and defend SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors and all their officers and employees, jointly and severally, against any and all claims and litigation and all damages, cost and expenses associated with such use:
 - ② Not impose any responsibility for any fault or negligence which may be cited in any such claim or litigation on SANYO ELECTRIC CO., LTD., its affiliates, subsidiaries and distributors or any of their officers and employees jointly or severally.
 - Information (including circuit diagrams and circuit parameters) herein is for example only; it is not guaranteed for volume production. SANYO believes information herein is accurate and reliable, but no guarantees are made or implied regarding its use or any infringements of intellectual property rights or other rights of third parties.